

# Frequency Synthesis



Patricia Desgreys

**ICS905 - FARE**


M2 « Integration Circuits & Systems »

# Summary

---


- Digital Transceiver RF Front-end
- RF oscillators
- PLLs
- Indirect frequency synthesis

# Transceiver chain

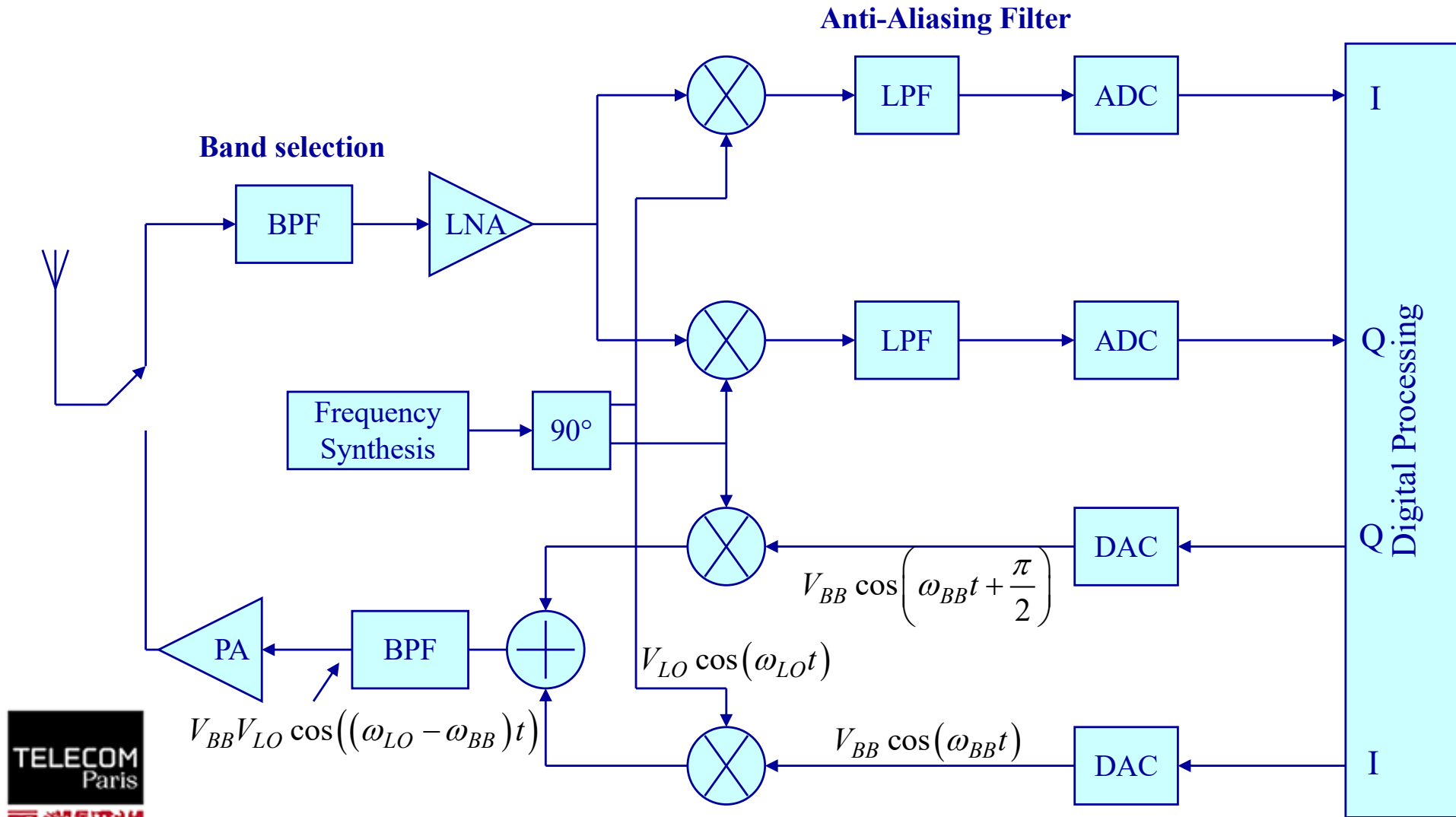

Direct conversion transceiver SSB

# Single-Side Band Transceiver

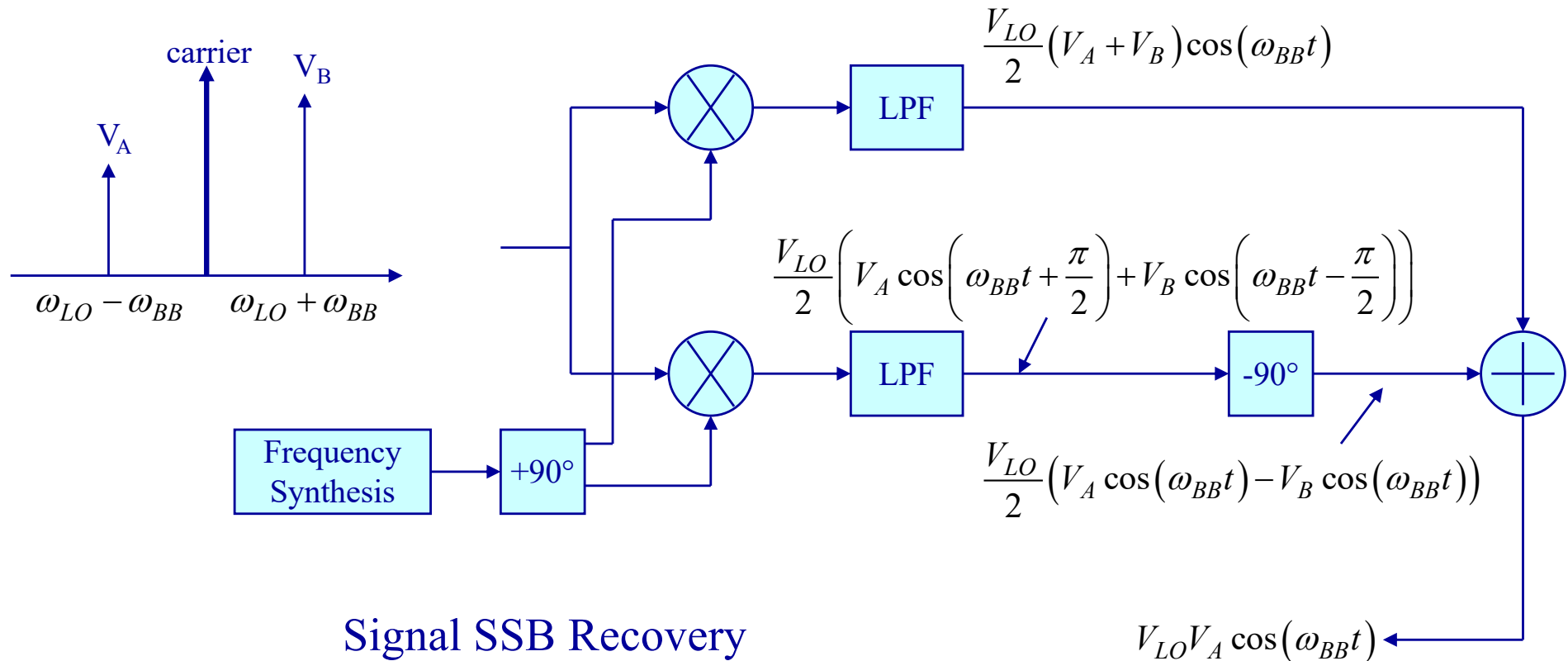

**RF frequency synthesis:** RF oscillator, PLL

$$f_{LO} = f_0 + k f_{ch}$$

Chanel selection

Mixer converts signal band around carrier frequency down to DC (baseband)

# Key functions

---

Almost all the functions are implemented in digital signals :

- Coding/decoding
- Modulation/demodulation (amplitude, frequency or phase)
- Pulses shaping (raised cosine filtering)


A few analog functions remain unavoidable :

- LNA, Mixers
- Power amplifiers
- Filters
- ADC & DAC
- RF oscillators
- PLLs
- Frequency synthesizers


 
# Frequency synthesizer

The “black box” view of a frequency synthesizer is a block getting a very stable reference frequency (usually provided by quartz oscillator) and delivering a set of frequencies between  $F_{\min}$  and  $F_{\max}$  with a resolution of  $\Delta f$  :




The frequency range  $[F_{\min}, F_{\max}]$  and the resolution  $\Delta f$  are synthesizer fundamental specifications which depend on the application.

 
# Main specifications

---


- Frequency range
- Resolution
- Accuracy
- Settling time
- Reference frequency
- Spurs
- Power consumption
- Temperature stability
- Phase noise



**Frequency Synthesis**

 

**Spur Rejection**

 

**Phase Noise**



**Settling Time**

# Summary

---

- Digital Transceiver RF Font-end



- RF oscillators


- PLLs

- Indirect frequency synthesis


 
# RF oscillators - Introduction

An oscillator must provide a self-sustaining periodic signal




Positive feedback system


$$V_s = \frac{H(j\omega)}{1 - G(j\omega)H(j\omega)} V_e$$

Barkhausen criterion

$$\begin{cases} |G(j\omega_0)| |H(j\omega_0)| = 1 \\ \arg\{G(j\omega_0)H(j\omega_0)\} = 0 \end{cases}$$

 


# RF oscillators – Output waveform

 


Input stage of an active CMOS mixer

 Mixer good behavior is favored if the waveform of the local oscillator (LO) exhibits abrupt transitions and if the duty cycle is equal to 50%




Ideal waveform = Square wave signal

 

Approximation of a square wave signal with a large amplitude sinusoid


- Large amplitude wave
- Differential topology for duty cycle of 50%

# RF oscillators – Frequency selection

 


The system oscillations frequency is determined by the characteristics of the selective circuit.

Frequency selective network or resonator

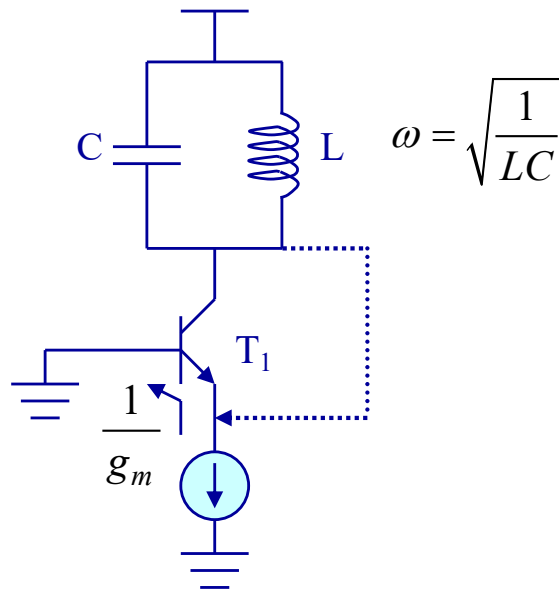


Direct return from collector to emitter

 

Colpitts oscillator


# RF oscillators – LC Architecture

 

Colpitts oscillator

Pros : High quality factor  
One single inductor

 Cons : Large ratio  $C_1/C_2$   
One terminal output



CMOS differential architecture

Pros : High quality factor  
Differential output



Cons : Matching of the two LC cells

# Voltage Controlled RF oscillators (VCO)


- Need to obtain an adjustable frequency RF oscillation for channel selection :

$$f_{LO} = f_0 + k f_{ch}$$

  - Frequency value controlled by a voltage



Use of a varicap diode in the LC cell

 

$$C_{\text{var}}(V_{\text{com}}) = \frac{C_0}{\left(1 - \frac{V_{\text{com}}}{V_{\text{diff}}}\right)^{\frac{1}{2}}}$$

# Voltage Controlled RF oscillators (VCO)

---

- VCO mathematical model

$$\omega_{LO} = \omega_{FR} + K_{VCO} V_{com} = \frac{d\Phi}{dt}$$

$$X(t) = V_{LO} \cos(\Phi) = V_{LO} \cos\left(\omega_{FR}t + K_{VCO} \int V_{com} dt\right)$$

- If the control voltage is constant, the frequency is shifted by  $K_{VCO} V_{com}$


$$V_{com} = V_0$$

$$X(t) = V_{LO} \cos\left((\omega_{FR} + K_{VCO} V_0)t + \phi_0\right)$$

- The VCO is a frequency modulator

$$V_{com} = V_m \cos(\omega_m t)$$
 
$$X(t) = V_{LO} \cos\left(\omega_{FR}t + \frac{K_{VCO}}{\omega_m} V_m \sin(\omega_m t)\right)$$



Rejection of the control voltage  
HF components

# RF oscillators – Phase noise



- Origin : internal noise of components constituting the oscillator  
example : amplifier thermal noise (use of a single transistor to minimize)
- Main effect : Random deviation of output wave frequency

$$X(t) = V_{LO} \cos(\omega_{LO}t + \Phi_n(t))$$

$\Phi_n(t)$  : phase noise

$$\text{si } |\Phi_n(t)| \ll 1, \quad X(t) \approx V_{LO} \{ \cos(\omega_{LO}t) - \Phi_n(t) \sin(\omega_{LO}t) \}$$

  
- Frequency domain characterization for RF applications :



$$L(\Delta\omega) = 10 \log \left( \frac{P_n}{P_{LO}} \right) \quad [dBc / Hz]$$
 
# Spectral characterization

- Thus, because of the different noise sources (thermal, 1/f...) the Power Spectral Density (PSD) spreads around  $f_0$





Example (DECT standard) : -97dBc/Hz @ 1,8 MHz



  
# Phase noise and Jitter

- Phase noise and jitter are two manifestations of a unique phenomenon : random fluctuations of the oscillator period.
- Phase noise is associated to spectral representation whereas jitter is associated to time representation of these fluctuations




# Phase noise – Reciprocal mixing

 


# Phase noise – Specification example

Real spectrum of the transmitter

 

 Adding noise during up-conversion to transmission



Calculation of a phase noise specification for the RF oscillator :

Bandwidth of interest :  $f_H - f_L = 30 \text{ kHz}$

Assumption :  $S_n(\Delta f)$  is constant in this band

$$S_n(\Delta f) = S_0 \quad [dBc / Hz]$$

What is the maximum value of  $S_0$  that guarantees an SNR in the channel of interest greater than 15 dB?

?

# Summary

---

- Digital Transceiver RF Font-end


- RF oscillators




- PLLs

- Indirect frequency synthesis

# PLL – Presentation

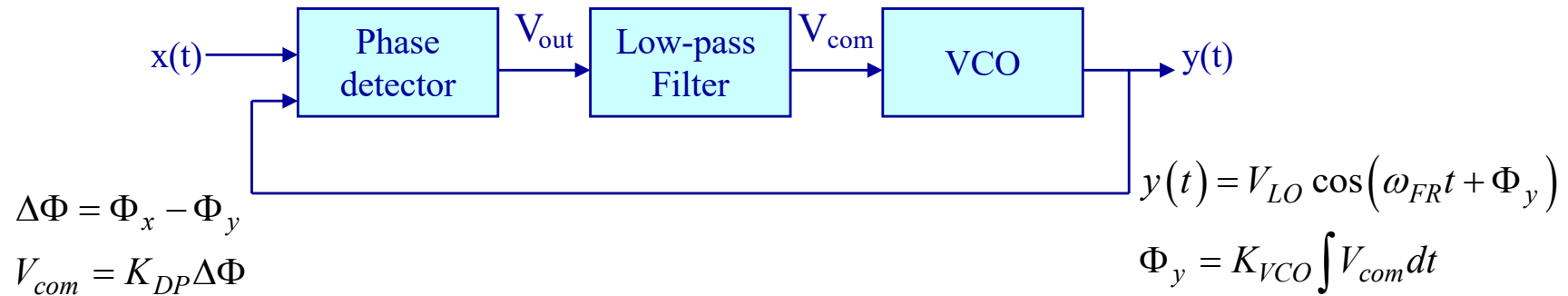

Basic Phase Locked Loop

 

PLL waveforms


The loop is locked when  $\Delta\Phi$  is constant, which corresponds to the equality of the input and output frequencies.

$$\omega_y = \omega_{FR} + K_{VCO}V_{com} = \omega_x$$

$$\Delta\Phi = \frac{V_{com}}{K_{DP}} = \frac{\omega_x - \omega_{FR}}{K_{DP} \cdot K_{VCO}}$$


**The frequency are exactly equal !**

# PLL – Dynamic behavior

 

Closed loop transfer function:  $H(p) = \frac{\Phi_y(p)}{\Phi_x(p)} = \frac{K G_{LPF}(p)}{p + K G_{LPF}(p)}$  avec  $K = K_{DP} K_{VCO}$

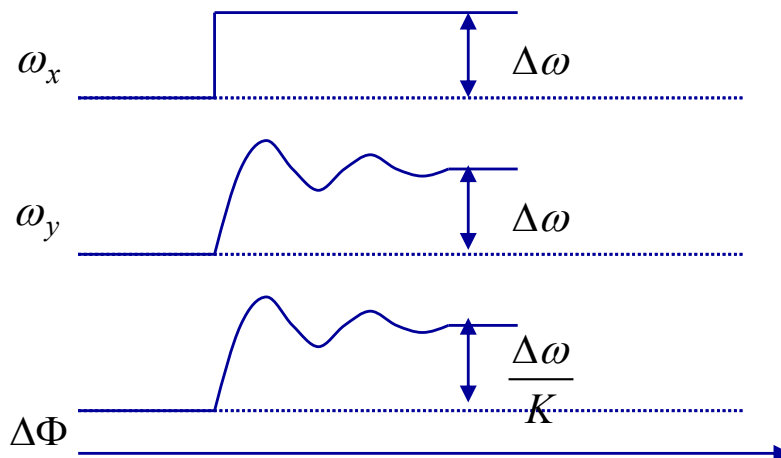with first order low-pass filter:  $G_{LPF}(p) = \frac{1}{1 + \frac{p}{\omega_{LPF}}}$ , we obtain a classical second order system:




$$H(p) = \frac{\omega_n^2}{p^2 + 2\zeta\omega_n p + \omega_n^2}$$

$$\text{avec } \omega_n = \sqrt{\omega_{LPF} K}$$


$$\text{et } \zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K}}$$

# Charge Pump PLL

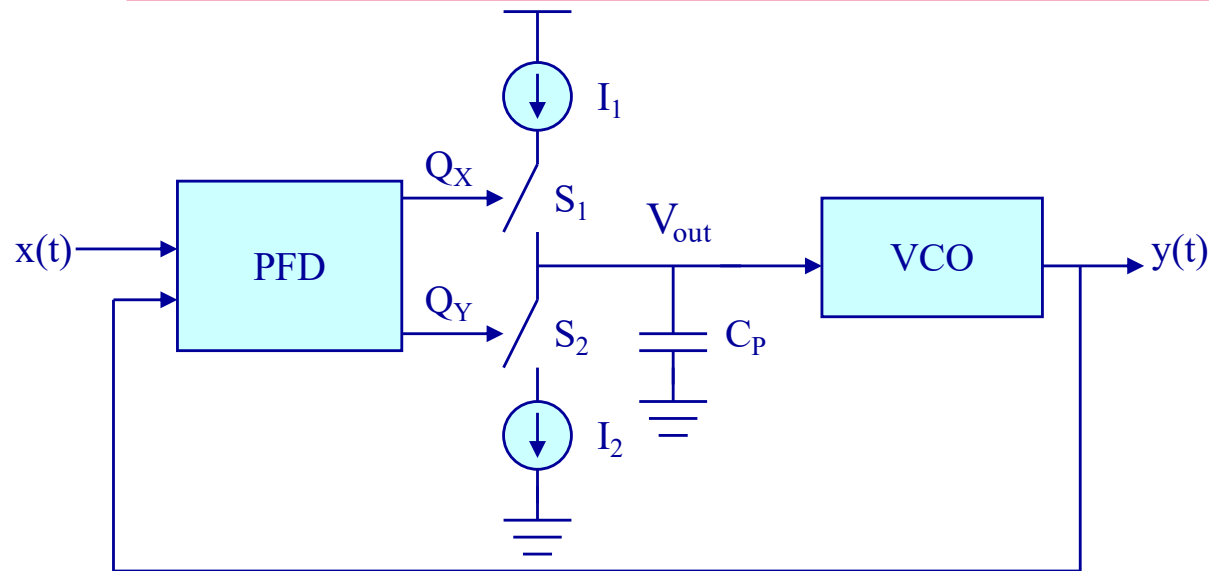

Architecture with 3-state  
phase/frequency detector and  
charge pump circuit

$$I_1 = I_2 = I$$

 

Waveforms in CPPLL  
with  $\omega_x > \omega_y$  in closed loop :

$$V_{out} = \text{const} \tan t$$


$$\omega_y = \omega_{FR} + K_{VCO} V_{out} = \omega_x$$

$$\Delta\Phi = \Phi_x - \Phi_y = 0$$

$$Q_X = Q_Y = 0$$
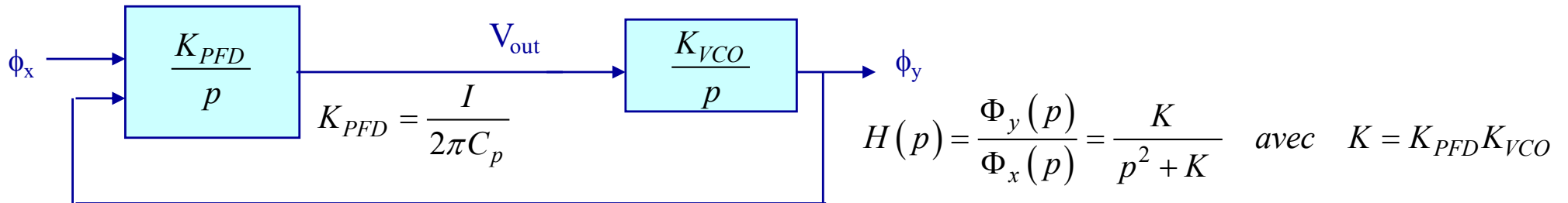
# Charge Pump PLL

Assuming that the bandwidth of the loop is much lower than the input frequency:




Main difference : two poles at zero in open loop

Pros :

- Maximum extension of the capture range,
- Increase of the locking speed,
- Zero static phase error (if ideal circuits).

Cons :


- Instability issue

 



 
# CPPLL – Input phase noise filtering

Transfer function of a second-order CPPLL with a stabilization zero :



$$H(p) = \frac{\Phi_y(p)}{\Phi_x(p)} = \frac{\omega_n^2 \left(1 + p/\omega_z\right)}{p^2 + 2\zeta\omega_n p + \omega_n^2}$$
 
$$\text{avec } \begin{cases} \omega_n^2 = K = K_{PFD} K_{VCO} \\ \omega_z = 1/RC_p \end{cases}$$




$$\Phi_x = \phi_0 + \Phi_n(t)$$

$\Phi_n(t)$  : phase noise


$$\Phi_y = \phi_0 + \Phi_{out}(t)$$

- Slow variations of the phase noise are reproduced at the output.
- HF noise is eliminated at the output.

# CPPLL – VCO phase noise filtering

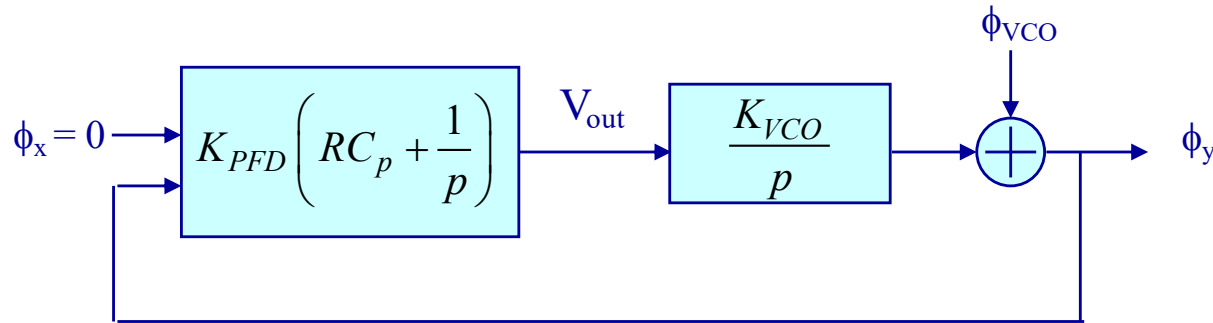
 
$$\frac{\Phi_y(p)}{\Phi_{VCO}(p)} = \frac{p^2}{p^2 + 2\zeta\omega_n p + \omega_n^2}$$



$$\Phi_{VCO} = \Phi_n(t)$$

$\Phi_n(t)$  : phase noise


$$\Phi_y = \Phi_{out}(t)$$

● The transfer function is a high-pass filtering

● An increase in the bandwidth of the PLL decreases the phase noise of the VCO

# PLL – Applications


## RF signal demodulation

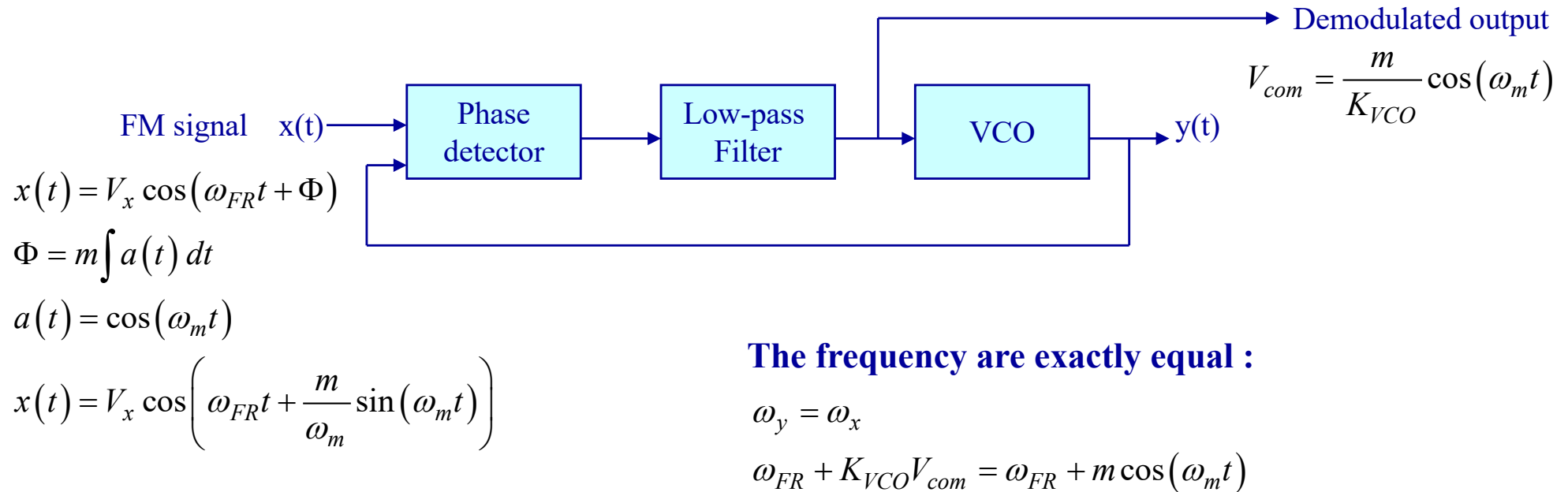

**Important: Loop bandwidth large enough !**

# PLL – Applications


## RF signal demodulation

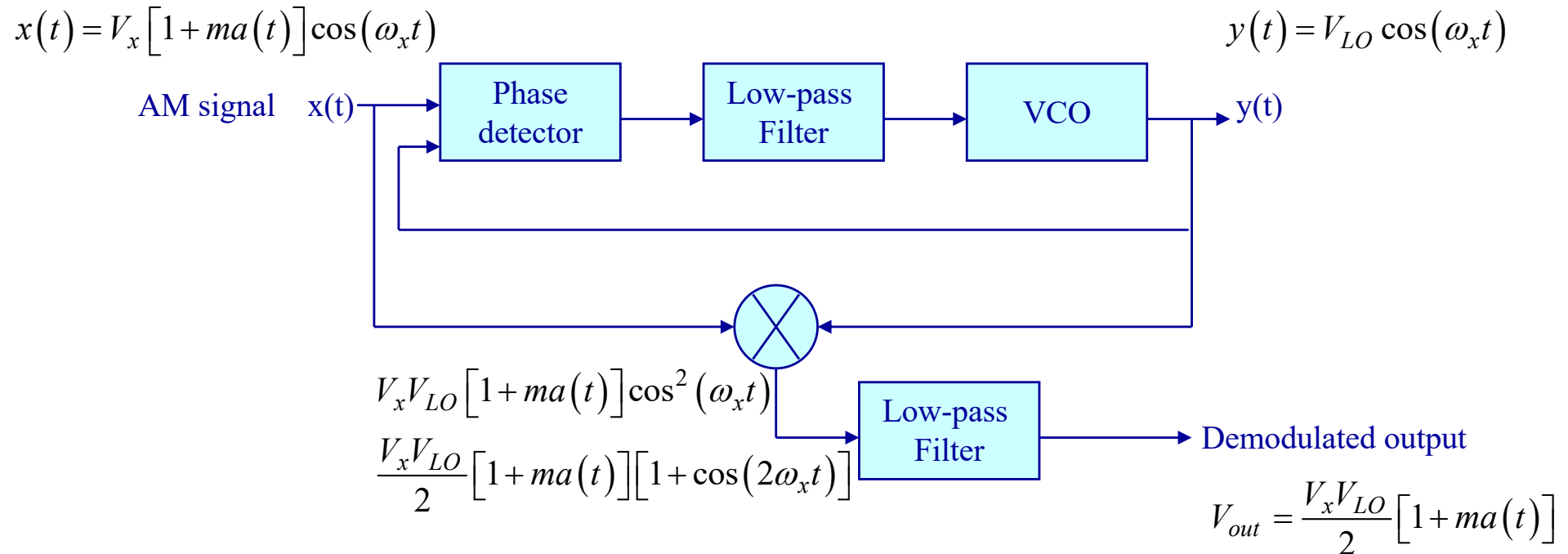


*Phase-locked loop for AM coherent demodulator*

# PLL – Applications

## Clock recovery

 


Manchester  
code (biphase)

 

Unipolar RZ  
code

Differential  
Biphase code  
(DBP)

 

**Important : Phase noise small enough !**

*Phase-locked loop for clock recovery from an encoded signal*

# PLL - Conclusion


---

Phase locked loops are key elements in digital communications systems. Their design and optimization are complex ( trade-off between speed, precision, stability).

Main features are :

- Locking and Capture Ranges
- Agility (locking speed)
- Phase noise
- Bandwidth
- Settling time

Major application for the RF front end

 

RF frequency synthesis : RF oscillator, PLL

$$f_{LO} = f_0 + k f_{ch}$$

Channel selection




# Summary

---

- Digital Transceiver RF Font-end
- RF oscillators
- PLLs


➡ ● Indirect frequency synthesis

# Frequency multiplication

 


$$\frac{y}{x} = \frac{H}{1 + \beta H} = \frac{1}{\beta}$$

Basic loop system

 

Voltage amplifier

 


$$\frac{f_{out}}{f_{in}} = M$$

Frequency multiplier



# Integer Modulus Synthesizer

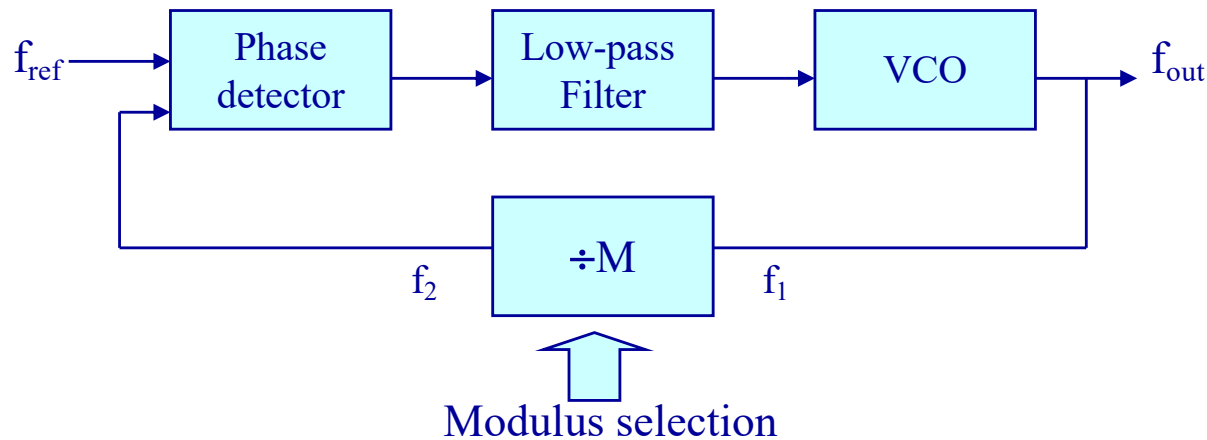


$$f_{out} = Mf_{ref} = f_0 + kf_{ch}$$

$$M_L \leq M \leq M_H$$

$$f_0 = M_L f_{ref}$$

$$f_{ch} = f_{ref}$$

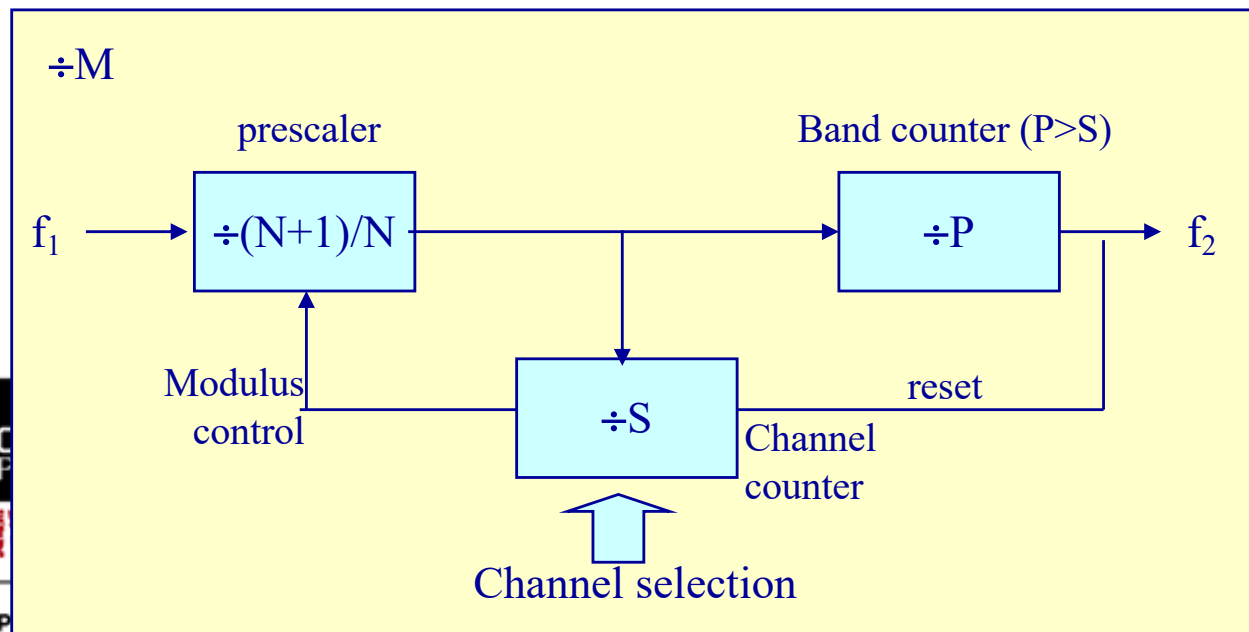The reference input frequency must be equal to the channel spacing.





Frequency divider  
by pulse counting

One output cycle occurs at the end of  $(N + 1) * S + N * (P - S)$  input cycles.

$$f_2 = \frac{f_1}{NP + S}$$

# Integer Modulus Synthesizer

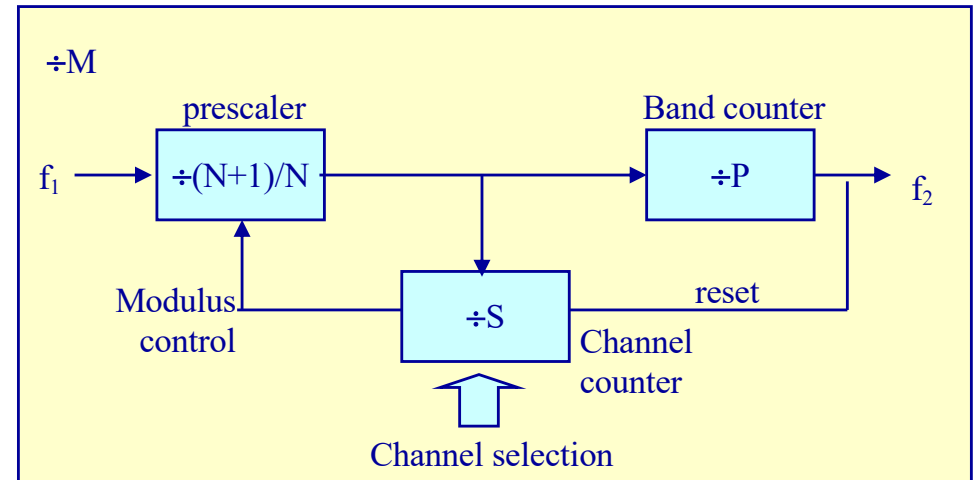 

- *Main advantage:* architecture simplicity

- *Implementation* in RF system :

Band counter, channel counter, PFD, charge pump

- *Main drawback:*

The reference frequency has a small value.  
The bandwidth of PLLs is limited to 1/10 of the input frequency to ensure stability

VCO  
prescaler


a single die in  
deeply submicronic  
CMOS technology

The bandwidth of the loop is limited!

ex : GSM inter-channel spacing : 200kHz  
Settling time 100  $\mu$ s or more



# Fractional Modulus Synthesizer

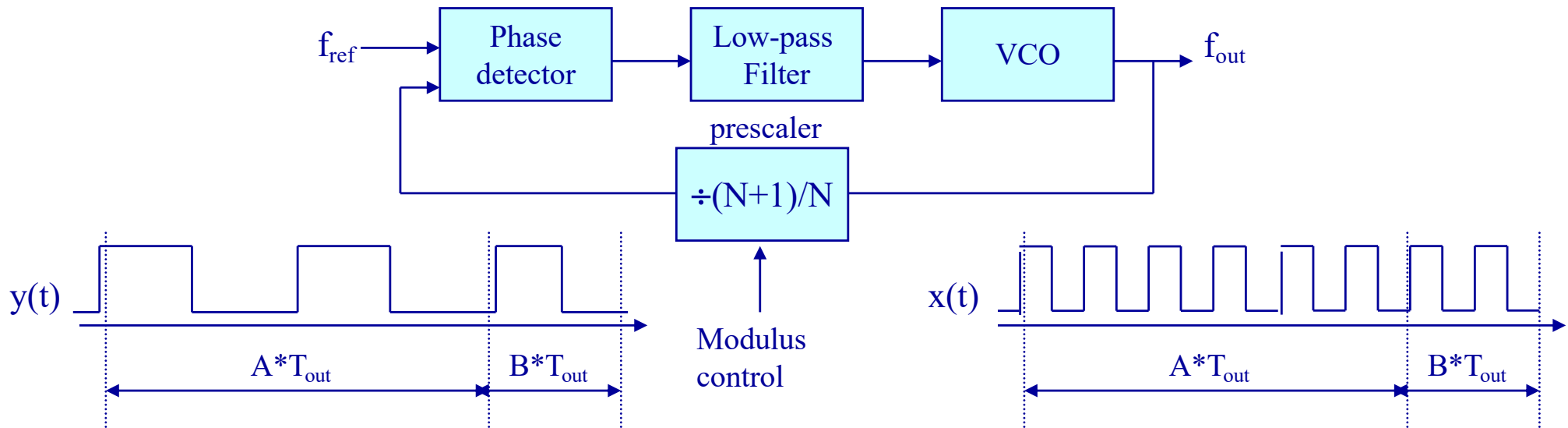

Number of pulses during the time  $(A+B)T_{out}$  :  
 $A/(N+1) + B/N$

'Average' or equivalent frequency of  $y(t)$  :  
 $(A/(N+1) + B/N) / ((A+B) T_{out})$   
 $= f_{out} / M$

Locked loop :

$$f_{ref} = f_{out} / M$$

$$f_{out} = M * f_{ref}$$

$$M = \frac{A+B}{\frac{A}{N+1} + \frac{B}{N}}$$


$$N < M < N+1$$



Use of a two-modulus  
frequency divider



# Fractional Modulus Synthesizer

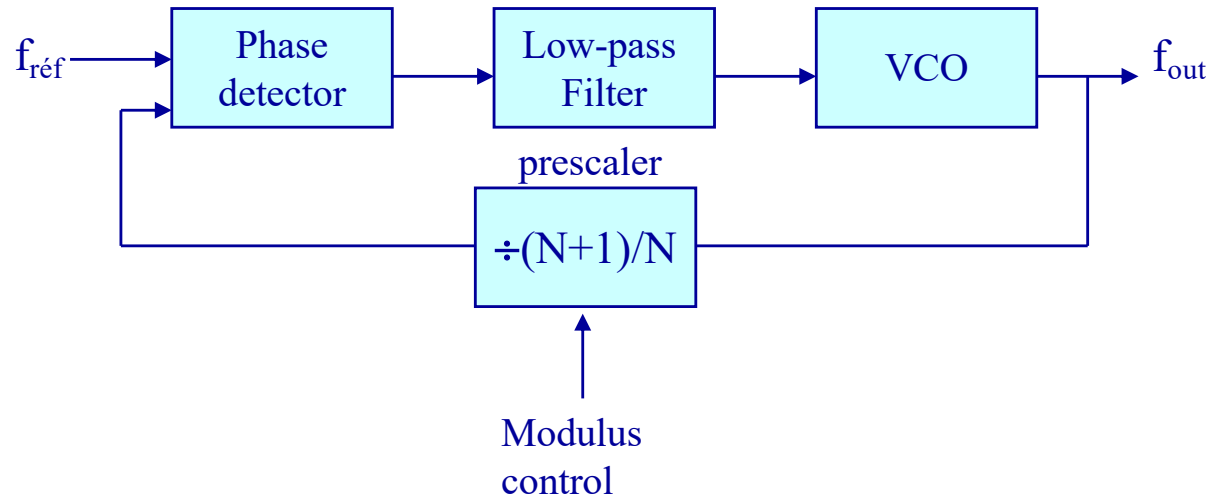

EXAMPLE :

Let's Consider a synthesizer for which the reference frequency is provided by a 1MHz oscillator. The expected output frequency is:

$$f_{out} = f_0 + kf_{ch}$$

with  $f_0=10$  MHz and  $f_{ch}=100$ kHz for  $k= 0, 1, 2, \dots, 9, 10$ .

What is the value of N?

What are the minimum possible values for A and B to address the different channels?

?